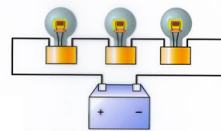


## Circuit Symbols

Series and Parallel Circuits  
Class Demonstration

## Series Circuits




For series circuits, the voltage across each resistor is additive:

$$V = V_1 + V_2 + V_3 + \dots$$

Current is constant throughout the circuit.

## Concept of Equivalent Resistance Equivalent Resistance for Series Circuits

## Parallel Circuits

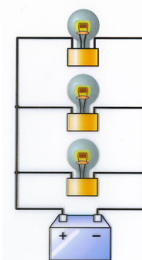

(b)

For parallel circuits, the current flowing through each branch is additive:

$$I = I_1 + I_2 + I_3 + \dots$$

The current flowing into a junction must equal the current flowing out of the junction.

Voltage is constant across each branch.


**Equivalent Resistance for Parallel Circuits**

**Examples**

### Combination Series and Parallel Circuits

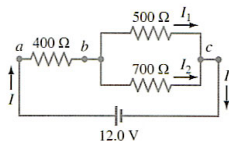
#### Example 19-4 pg. 526

How much current flows from the battery shown in the circuit?



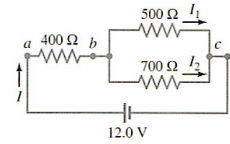
#### Example 19-4 pg. 526

How much current flows through the 500 Ω resistor shown in the circuit?



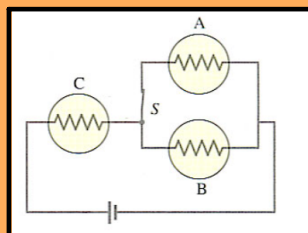
### Concept Check:

When the switch "S" is closed, how will the brightness of bulbs A and B compare with that of C? What happens when the switch is open?


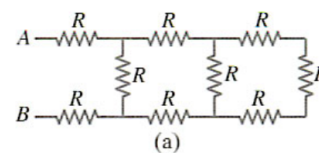
### Resistor Ladders

Estimate the equivalent resistance of the resistor ladder.



## EMF ( $\mathcal{E}$ ) and Terminal Voltage



### Example 19-7 pg. 528

A 9.0V battery whose internal resistance  $r$  is  $0.50\ \Omega$  is connected in the circuit shown.

How much current is drawn from the battery?

What is the terminal voltage of the battery?

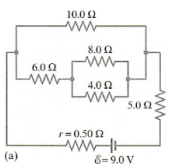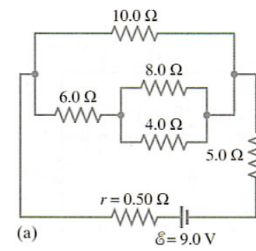What is the current in the  $6.0\ \Omega$  resistor?



**Circuits:  
Verifying Ohm's Law**



## Kirchhoff's Rules

**Junction Rule:** at any point, the sum of all the currents entering the junction must equal the sum of all the currents leaving the junction.

**Loop Rule:** the sum of all the changes in potential around any closed path of a circuit must be zero.


**NOTE:** If a branch contains a battery, always assign the direction of "I" consistent with the definition of current flow.

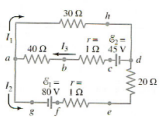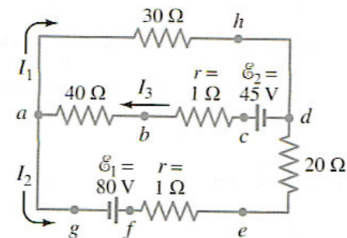**Example 19-8 pg. 530 Using Kirchhoff's Rules**  
Calculate  $I_1$ ,  $I_2$ , and  $I_3$




EMF's in Series  
Battery Chargers

## Capacitors in Circuits

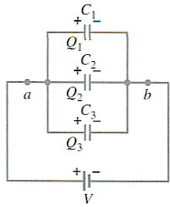


(a)  $C = C_1 + C_2 + C_3$

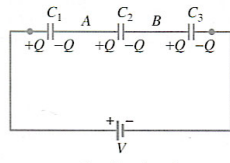


(b)  $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$
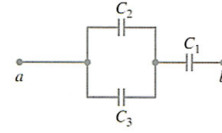
## Example 19-10 pg. 534

Determine the capacitance in terms of  $C$ :



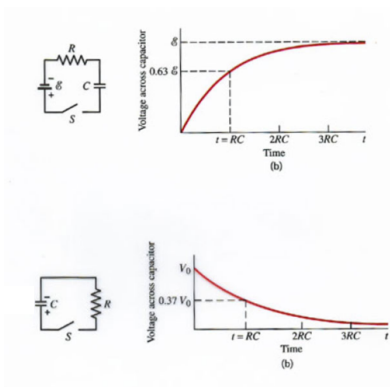
## Capacitors and Resistors in circuits together; the R-C Circuit



Example of an R-C circuit:


The Heart Pacemaker

## Electrical Hazards: Current Leakage

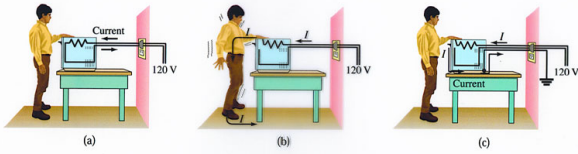

© 1998 by Prentice-Hall, Inc.  
A Simon & Schuster Company  
Upper Saddle River, New Jersey 07075

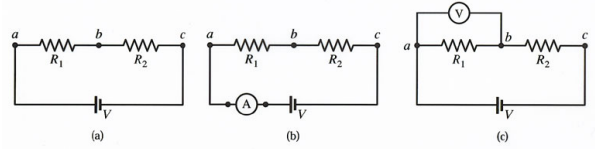© 1998 by Prentice-Hall, Inc.  
A Simon & Schuster Company  
Upper Saddle River, New Jersey 07075



## Electrical Meters